

# Low Power Design – An Emerging Discipline

Historical figure of merit for VLSI design –performance (circuit speed) and chip area (circuit density/cost)

Power dissipation is now an important metric in VLSI design

- No single major source for power savings across all design levels – Required a new way of THINKING!!!  
Companies lack the basic power-conscious culture and designers need to be educated in this respect
- Overall Goal – To reduce power dissipations but maintaining adequate throughput rate

# Need for Low Power VLSI Chips

Power dissipation **was** neglected due to

- Low device density
- Low operating frequency
- **Now** it is important issue due to
  - High device density
  - High operating frequency
  - Proliferation of portable consumer electronics
  - Concerns on Environments and energy sources

## Competitive Reasons – Low Power


- **Battery Powered Systems** – Extended Battery Life and reduce weight and size.
- **High-Performance Systems**
  - Cost
- **Package** (chip carrier, heat sink, card slots, plenum,)

- **Power Systems** (supplies, distribution, regulators, ...)
- **Fans** (noise, power, reliability, area, ...)
- **Operating cost to customer** – Energy Star issue.
- **Reliability**
- **Failure rate increase** by 4X for  $T_j$  @ 110C vs 70C
- Mission critical operation at 100C
- **Size and Weight** – Product footprint (office and desk space).
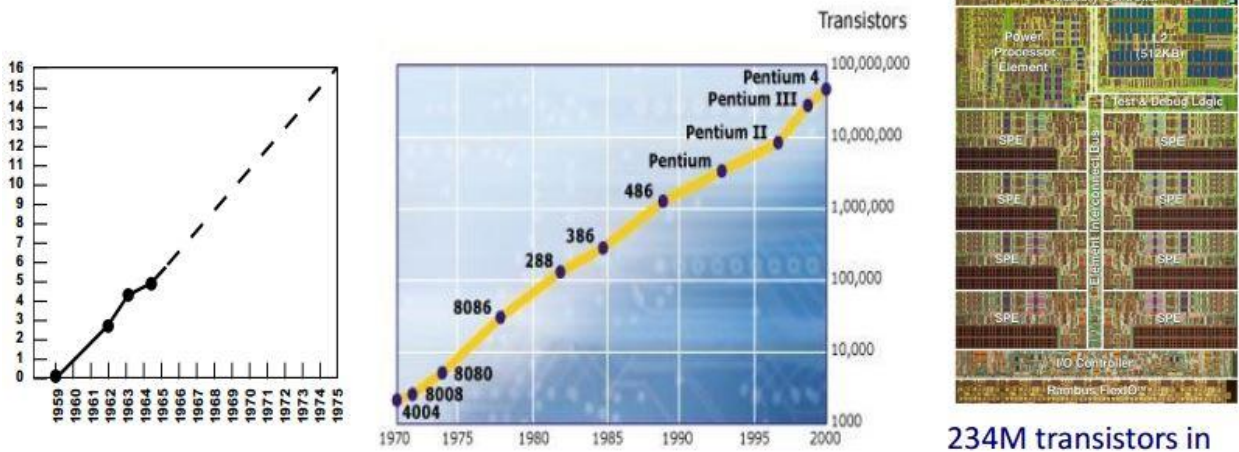
## Moore's Law

- In 1965, Gordon Moore noted that the number of transistors on a chip doubled every 18 to 24 months.

- He made a prediction that semiconductor technology will double its effectiveness every 18 months




## Unit 3: Probabilistic Power Analysis Methods
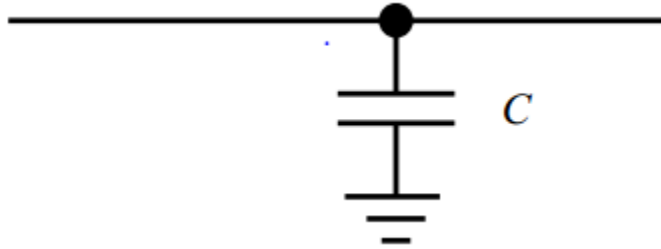
### Basic Idea

- View signals as a random processes


- $\text{Prob}\{s(t) = 1\} = p_1$   
 $p_0 = 1 - p_1$



0→1 transition probability =  $(1 - p_1) p_1$

Power,  $P = (1 - p_1) p_1 CV^2 f_{ck}$

## Source of Inaccuracy

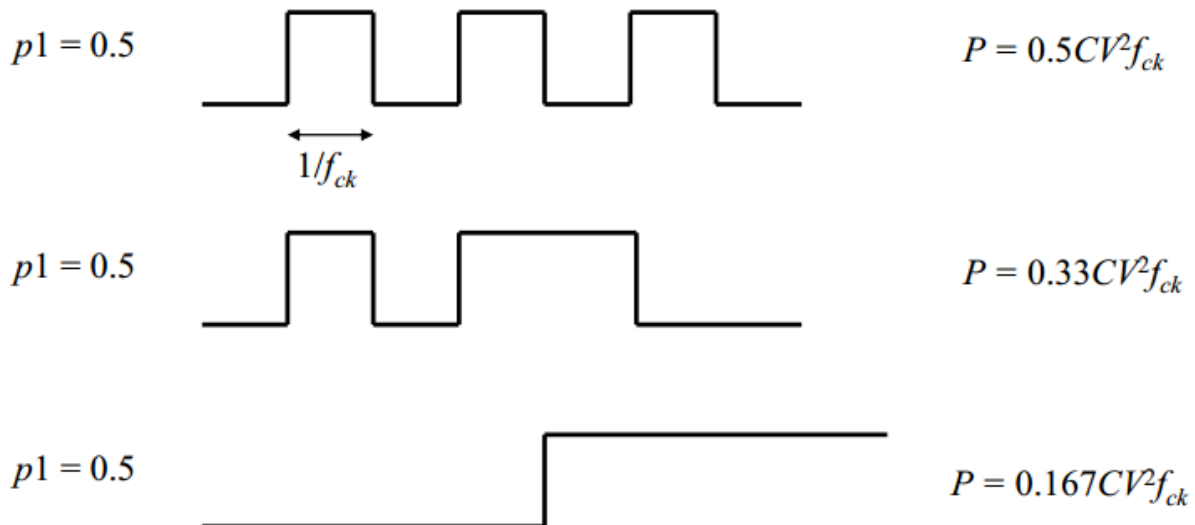

Observe that the formula, Power,  $P = (1 - p_1) p_1 CV 2f_{ck}$ , is not correct

## Switching Frequency

Number of transitions per unit time:

$$T = \frac{N(t)}{t}$$

*For a continuous signal:*

$$T = \lim_{t \rightarrow \infty} \frac{N(t)}{t}$$

T: is defined as the transition density

## Static Signal Probabilities

Observe signal for interval  $t_0 + t_1$


– Signal is 1 for duration  $t_1$

- Signal is 0 for duration  $t_0$
- Signal probabilities:
  - $p_1 = t_1/(t_0 + t_1)$
  - $p_0 = t_0/(t_0 + t_1) = 1 - p_1$

## Static Transition Probabilities


- Transition probabilities:
  - $T_{01} = p_0 \text{ Prob}\{\text{signal is 1} \mid \text{signal was 0}\} = p_0 p_1$
  - $T_{10} = p_1 \text{ Prob}\{\text{signal is 0} \mid \text{signal was 1}\} = p_1 p_0$
  - $T = T_{01} + T_{10} = 2 p_0 p_1 = 2 p_1 (1 - p_1)$
- Transition density:  $T = 2 p_1 (1 - p_1)$
- Transition frequency:  $f = T/2$
- Power =  $CV^2T/2$  (correct formula)

## Static Transition Frequency

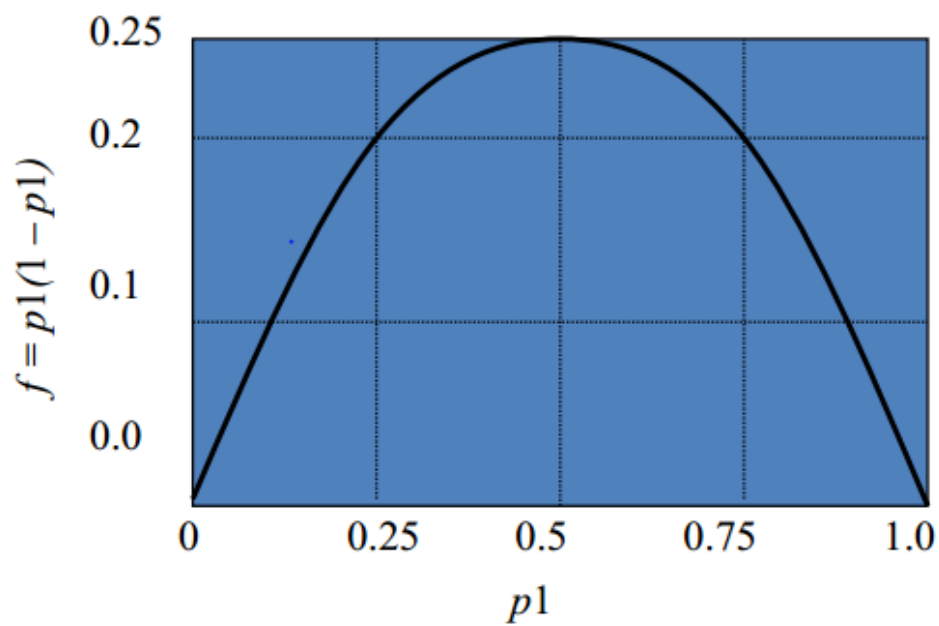

Inaccuracy in Transition Density



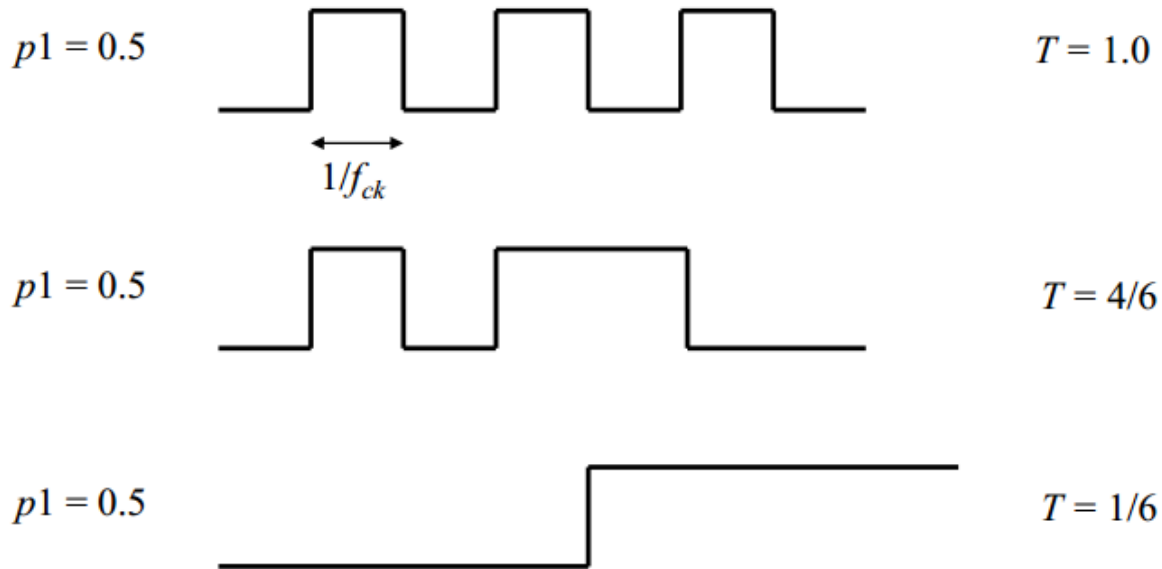

Observe that the formula,  $T = 2 p1 (1 - p1)$ , is not correct.

## Cause for Error and Correction

- Probability of transition is not independent of the present state of the signal
- Consider probability  $p01$  of a  $0 \rightarrow 1$  transition,
- Then  $p01 \neq p0 p1$
- We can write  $p1 = (1 - p1)p01 + p1 p11$

$$p1 = \frac{p01}{1 - p11 + p01}$$

## Correction (Cont.)


- Since  $p_{11} + p_{10} = 1$ , i.e., given that the signal was previously 1, its resent value can be either 1 or 0,

Therefore,

$$p_1 = \frac{p_{01}}{p_{10} + p_{01}}$$

This uniquely gives signal probability as a function of transition probabilities.

## Transition and Signal probabilities

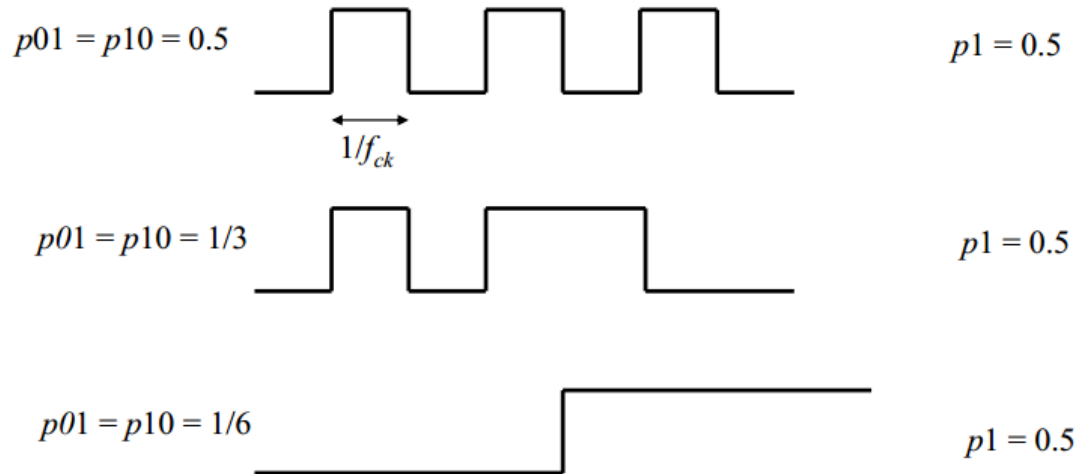

Probabilities:  $p_0$ ,  $p_1$ ,  $p_{00}$ ,  $p_{01}$ ,  $p_{10}$ ,  $p_{11}$

- $p_{01} + p_{00} = 1$
- $p_{11} + p_{10} = 1$
- $p_0 = 1 - p_1$

$$p_1 = \frac{p_{01}}{p_{10} + p_{01}}$$




Transition Density

- $T = 2 p_1(1 - p_1) = p_0 p_{01} + p_1 p_{10}$   
 $= 2 p_{10} p_{01} / (p_{10} + p_{01})$   
 $= 2 p_1 p_{10} = 2 p_0 p_{01}$


## Power Calculation

- Power can be estimated if transition density is known for all signals.
- Calculation of transition density requires
  - Signal probabilities
  - Transition densities for primary inputs; computed from vector statistics

## Signal Probabilities

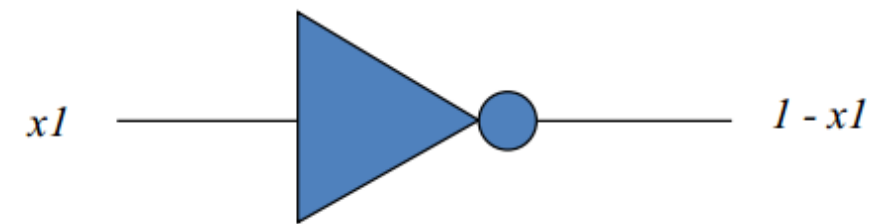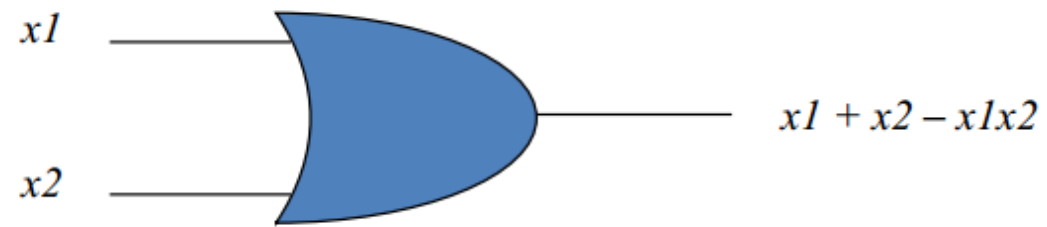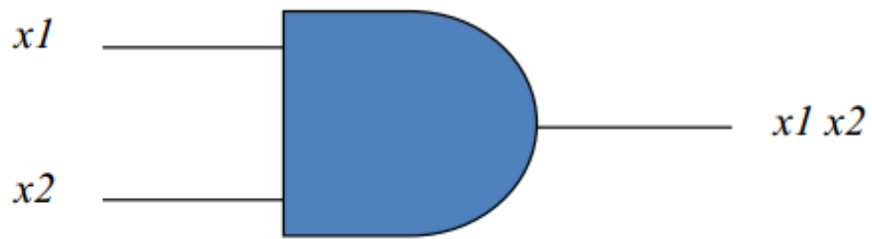

# Signal Probabilities

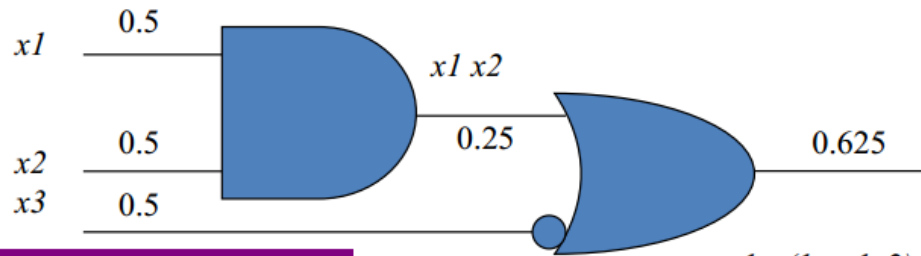


$x_1$	$x_2$	$x_3$	$y$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 y &= 1 - (1 - x_1 x_2) x_3 \\
 &= 1 - x_3 + x_1 x_2 x_3 \\
 &= 0.625
 \end{aligned}$$


**Ref: K. P. Parker and E. J. McCluskey,  
"Probabilistic Treatment of General**

# Correlated Signal Probabilities

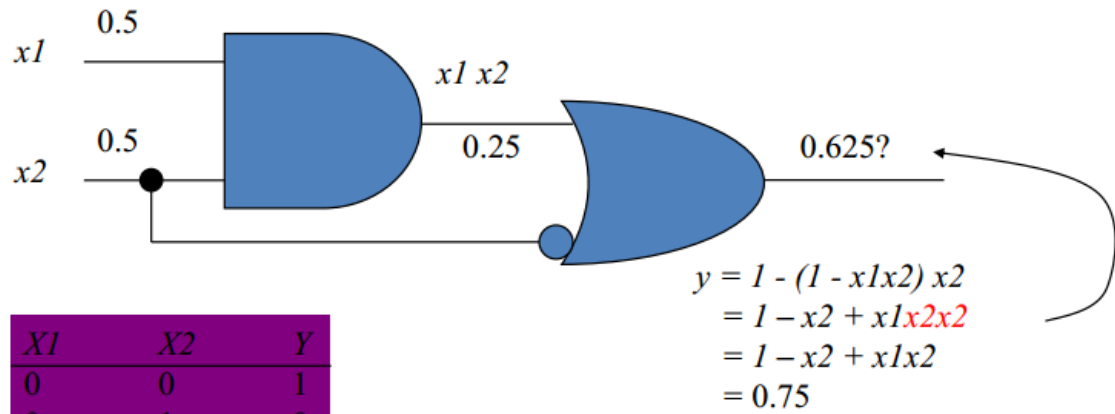

$x_1$	$x_2$	$Y$
0	0	1
0	1	0
1	0	1
1	1	1

# Correlated Signal Probabilities

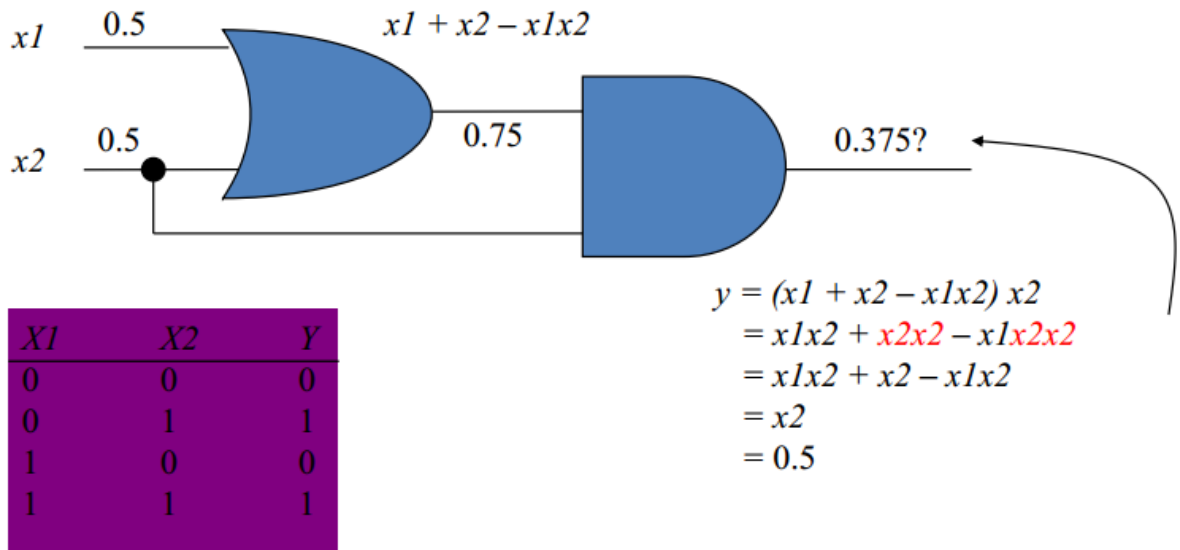

$$\begin{aligned}
 y &= (x_1 + x_2 - x_1x_2) x_2 \\
 &= x_1x_2 + \textcolor{red}{x_2x_2} - x_1x_2x_2 \\
 &= x_1x_2 + x_2 - x_1x_2 \\
 &= x_2 \\
 &= 0.5
 \end{aligned}$$

## Observation

- Numerical computation of signal probabilities is accurate for fan out-free circuits.

## Remedies

- Use Shannon's expansion theorem to compute signal probabilities.
- Use Boolean difference formula to compute transition densities.



## Shannon's Expansion Theorem

- C. E. Shannon, "A Symbolic Analysis of Relay and Switching Circuits," *Trans. AIEE*, vol. 57, pp. 713-723, 1938.
- Consider: Boolean variables,  $X_1, X_2, \dots, X_n$
- Boolean function,  $F(X_1, X_2, \dots, X_n)$
- Then  $F = X_i F(X_i=1) + X_i' F(X_i=0)$
- Where
- $X_i'$  is complement of  $X_i$
- Cofactors,  $F(X_i=j) = F(X_1, X_2, \dots, X_i=j, \dots, X_n)$ ,  $j = 0$  or  $1$


## Expansion about Two Inputs

- $F = X_i X_j F(X_i=1, X_j=1) + X_i X_j' F(X_i=1, X_j=0) + X_i' X_j F(X_i=0, X_j=1) + X_i' X_j' F(X_i=0, X_j=0)$

$X_j=0$ )

- In general, a Boolean function can be expanded about any number of input variables.
- Expansion about  $k$  variables will have  $2^k$  terms.

## Correlated Signal Probabilities

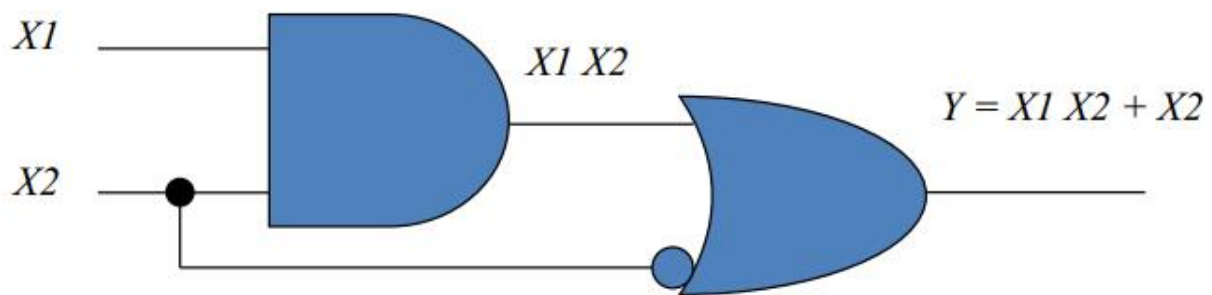

$X1$	$X2$	$Y$
0	0	0
0	1	0
1	0	0
1	1	1

Shannon expansion about the reconverging input:

$$\begin{aligned} Y &= X2 Y(X2=1) + X2' Y(X2=0) \\ &= X2 (X1) + X2' (1) \end{aligned}$$


## Correlated Signals

- When the output function is expanded about all reconverging input variables,
- All cofactors correspond to fan out-free circuits.
- Signal probabilities for cofactor outputs can be calculated without error.
- A weighted sum of cofactor probabilities gives the correct probability of the output.

- For two reconverging inputs:

$$f = x_i x_j f(X_i=1, X_j=1) + x_i (1-x_j) f(X_i=1, X_j=0) \\ + (1-x_i) x_j f(X_i=0, X_j=1) + (1-x_i)(1-x_j) f(X_i=0, X_j=0)$$

# Correlated Signal Probabilities

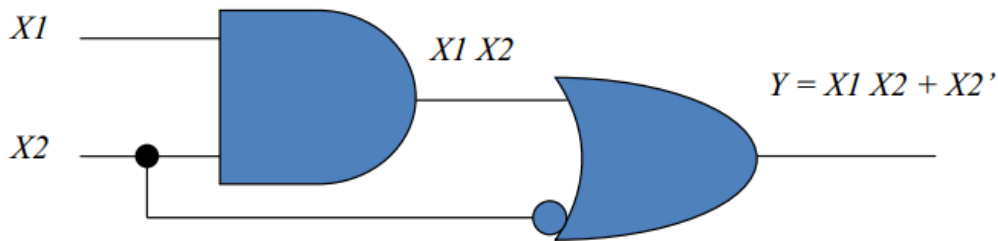


$X1$	$X2$	$Y$
0	0	1
0	1	0
1	0	1
1	1	1

Shannon expansion about the reconverging input:

$$Y = X2 Y(X2=1) + X2' Y(X2=0) \\ = X2 (X1) + X2' (1)$$

$$y = x2 (0.5) + (1-x2) (1) \\ = 0.5 (0.5) + (1-0.5) (1) \\ = 0.75$$


## Example

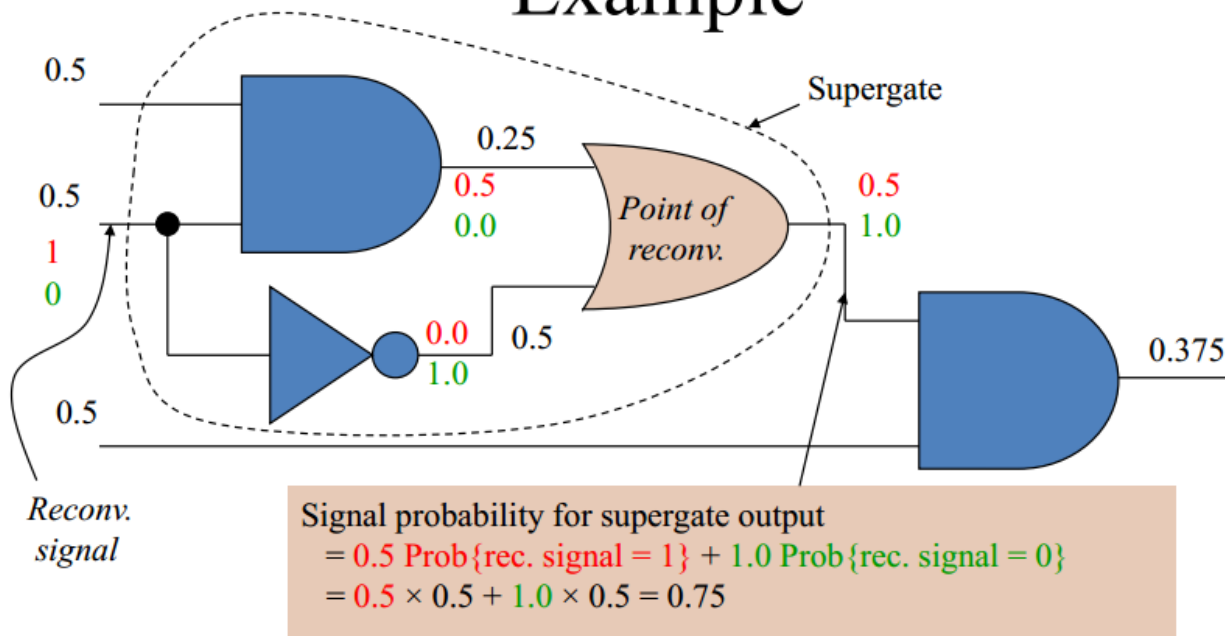
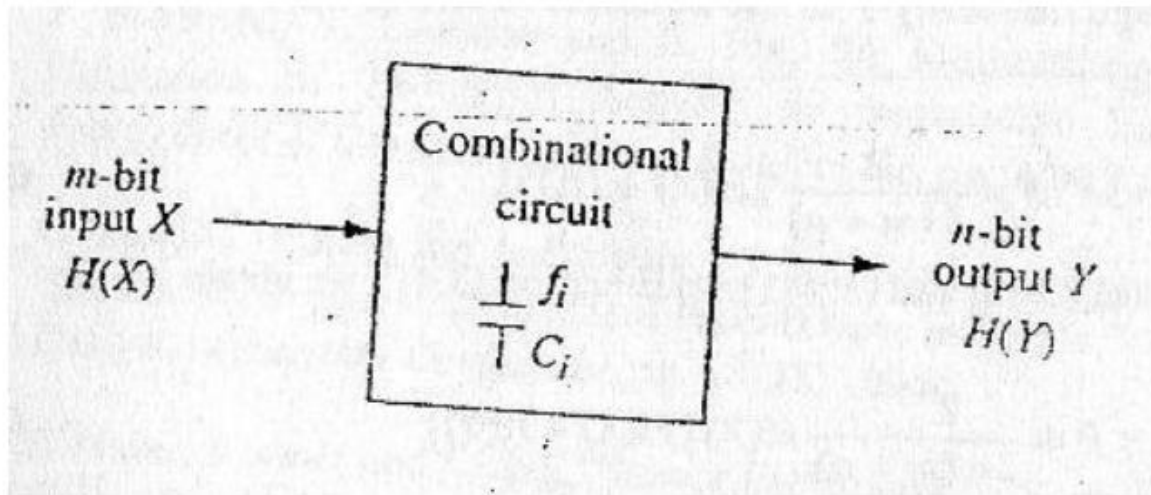
## Signal entropy

- The entropy of a set of logic signals is a measure of its randomness
- Entropy correlates to the average switching frequency of the signals
- Skewed occurrence probability gives a low probability measure
- If signal switching is active, it maximizes the entropy of the signals
- These observations prompts the idea of using signal entropy for power estimation.

Power estimation of combinational logic using entropy analysis



# Entropy

- Entropy based approach
  - Entropy: Measure of uncertainty in a random variable
  - Entropy  $H$  of a random variable  $x$  is given by

$$H(x) = p \log \frac{1}{p} + (1-p) \log \frac{1}{1-p}$$

- $p$ : probability of  $x$  being 1

- Recall that

$$P_{avg} \propto D_{avg} \cdot GE \cdot C_{avg}$$

- $D_{avg}$ : Average node switching activity
- $GE$ : Gate equivalents
- $C_{avg}$ : Average gate capacitance

- Hypothesis

- Can  $D_{avg}$  be estimated only from knowledge of inputs and output behavior?

- Answer: Yes!

$$P_{avg} \propto H.GE.C_{avg}$$


- Entropy  $H$  is given by

$$H \approx \frac{2/3}{n+m} (H(X) + H(Y))$$

- $H(X)$  and  $H(Y)$  are respectively the input and output entropies


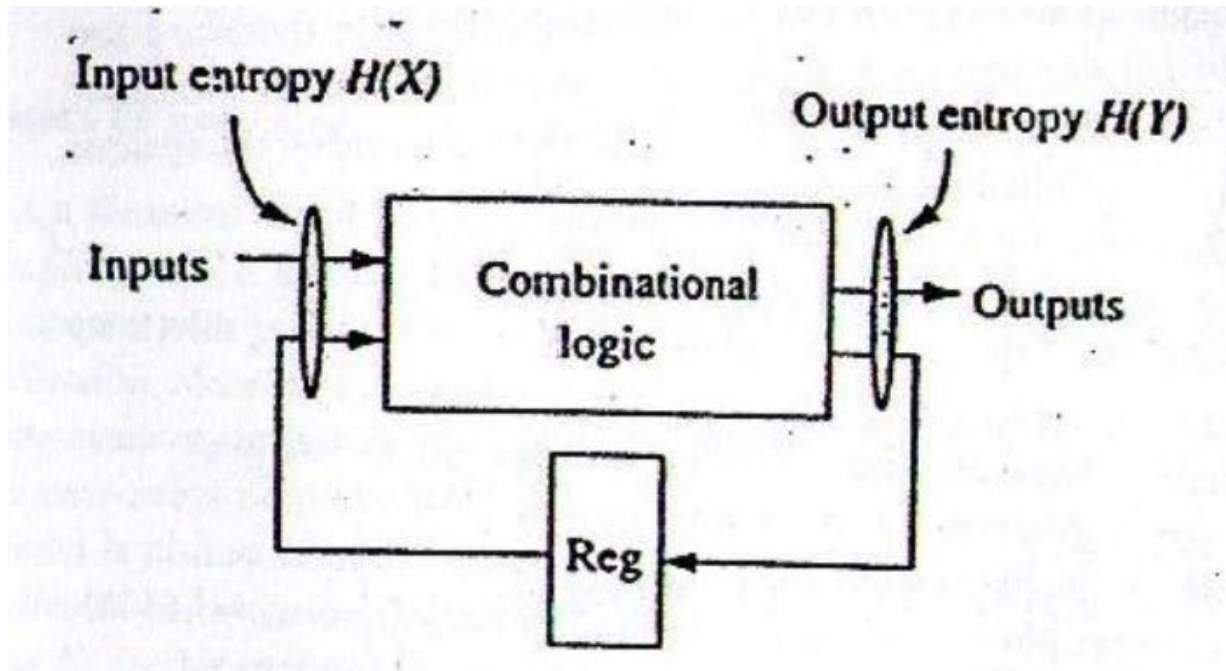
# Entropy analysis of a sequential circuit



## Entropy

- Entropy Based Power Estimation

Methodology:

- Run a structural RTL simulation to measure input/output entropies
- Using input/output entropies, estimate  $P_{avg}$

for the combinational block

- Use other techniques to estimate latch and clock power